

---

# Computer Science 141

## Computing Hardware

Fall 2009

Harvard University




Instructor: Prof. David Brooks

[dbrooks@eecs.harvard.edu](mailto:dbrooks@eecs.harvard.edu)
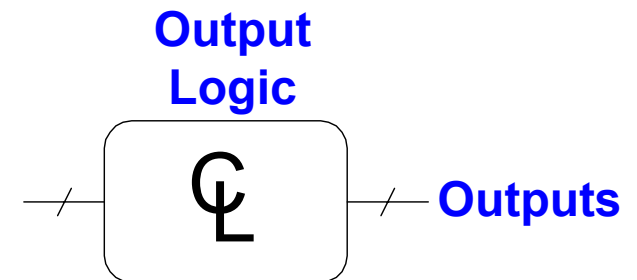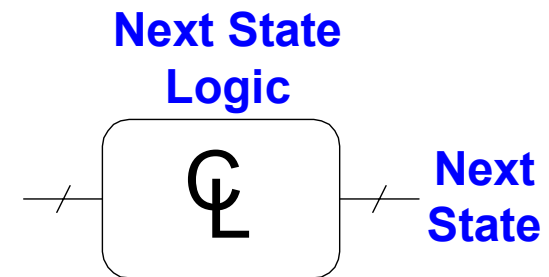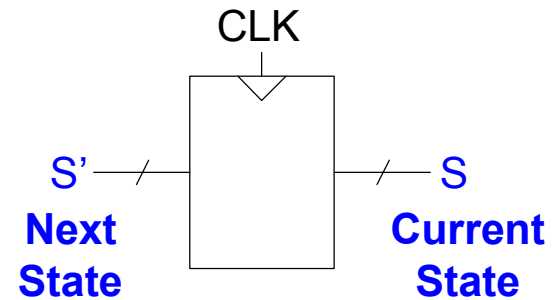
# Finite State Machine (FSM)

---


- Consists of:
  - State register that
    - Store the current state and
    - Load the next state at the clock edge
  - Combinational logic that
    - Computes the next state
    - Computes the outputs




# Moore vs. Mealy machines

---

- block diagrams


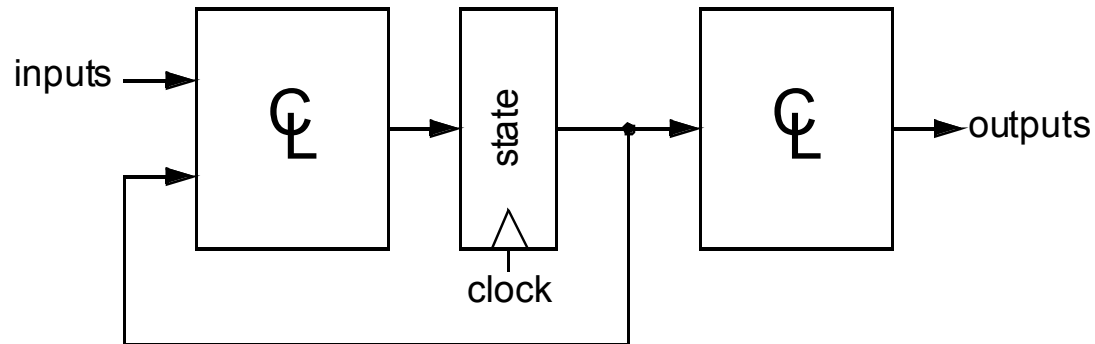


*Moore machine*

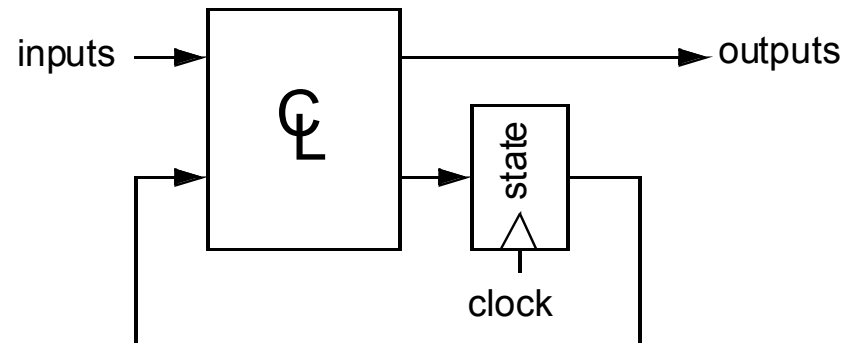

*Mealy machine*



# Moore Machine

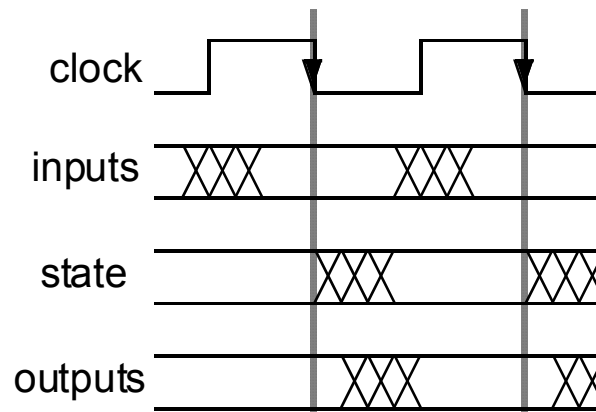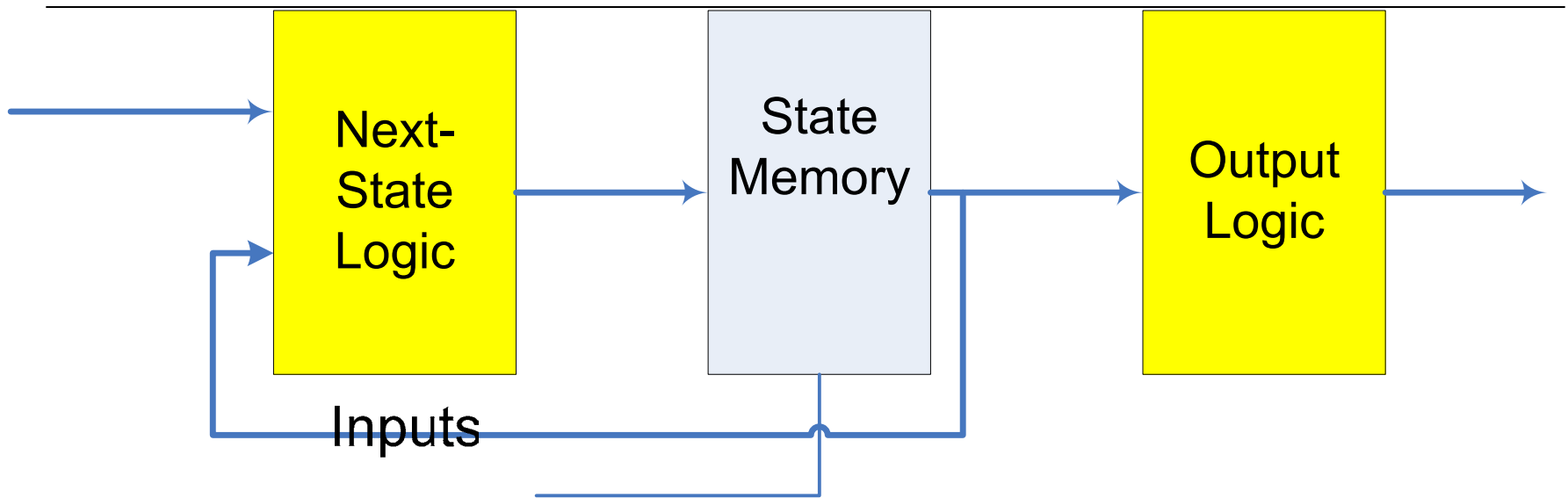

Excitation

*Moore machine timing*

# Mealy Machine

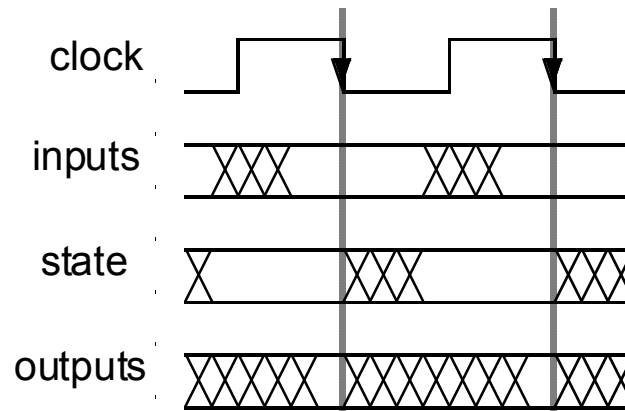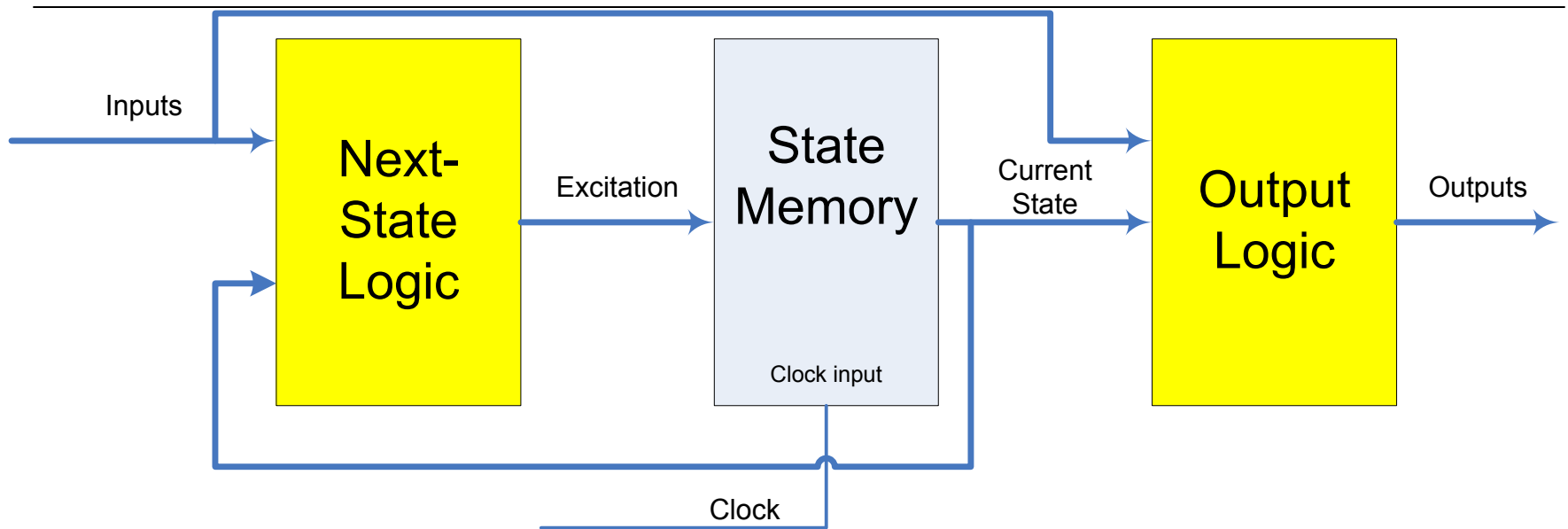


*Mealy machine timing*
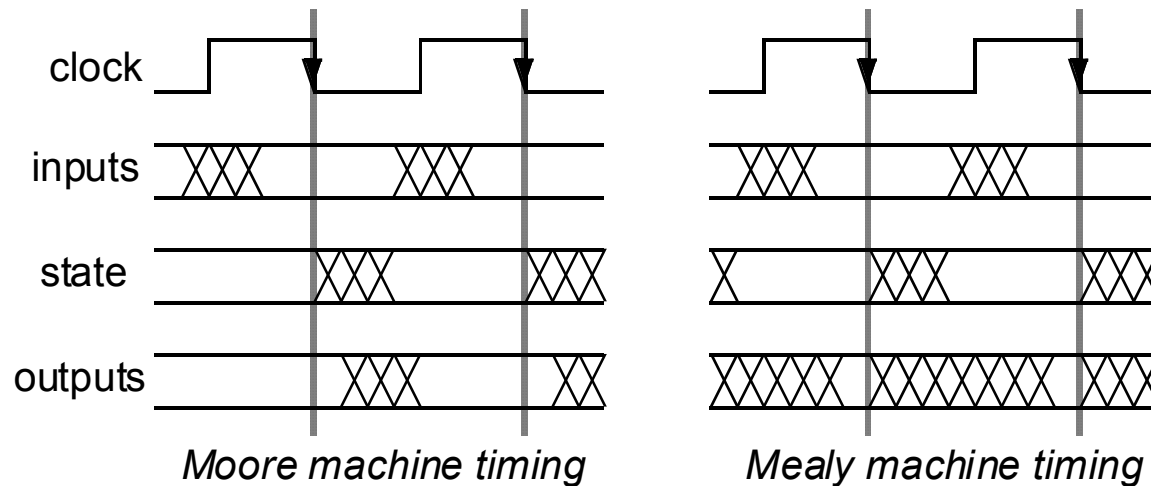
# Moore vs. Mealy machines


---

- timing of input, state, and output changes



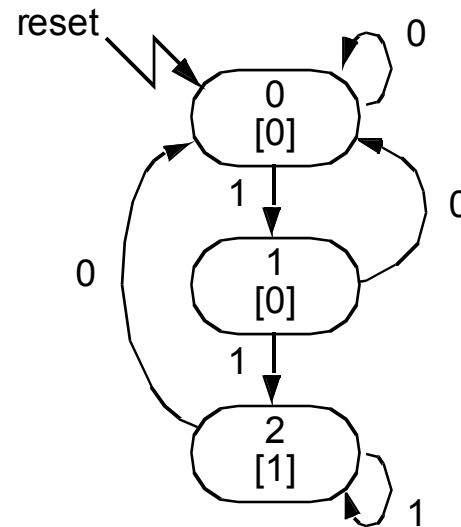
# Mealy vs. Moore: Design Example

- function: assert output if 2 or more 1's in a row
- state diagram:



*Moore machine*

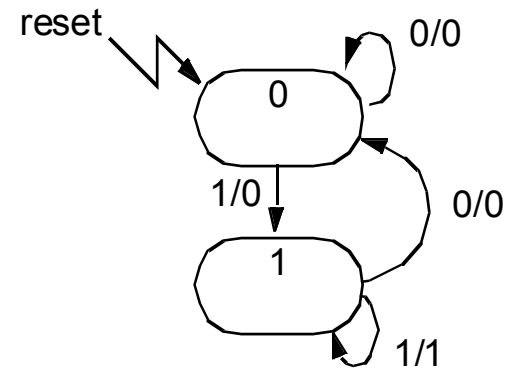


*Mealy machine*

- advantages/disadvantages
  - Mealy often has fewer states than Moore machine since it associates outputs with transitions
  - Mealy machine can fall victim to glitches since outputs are asynchronous
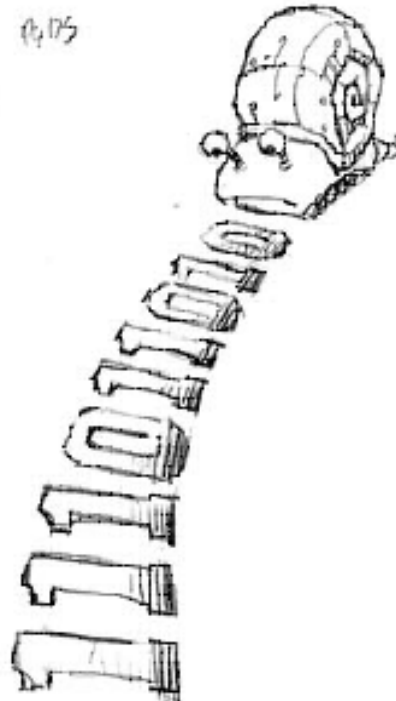
# Moore vs. Mealy FSM

---


- Alyssa P. Hacker has a snail that crawls down a paper tape with 1's and 0's on it. The snail smiles whenever the last four digits it has crawled over are 1101. Design Moore and Mealy FSMs of the snail's brain.



# State Transition Diagrams


---

Moore FSM

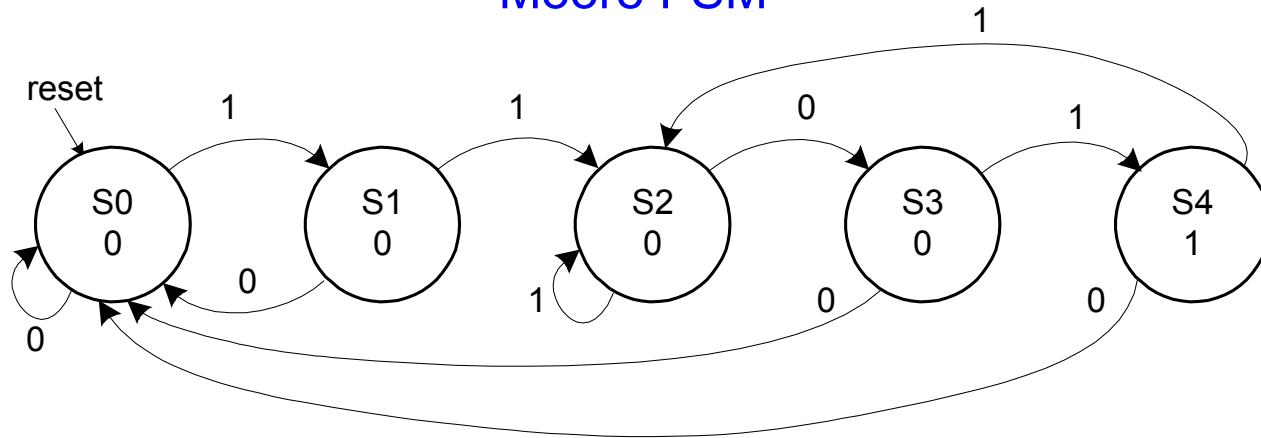

Mealy FSM: arcs indicate input/output

Mealy FSM

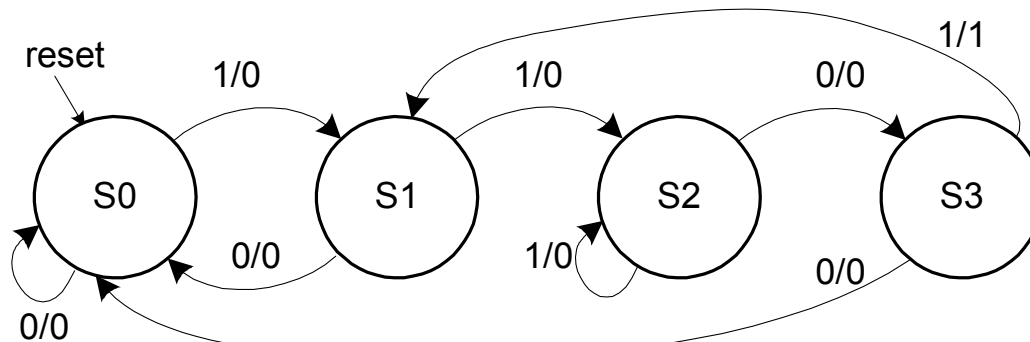

# Moore FSM State Transition Table

Current State			Inputs	Next State		
$S_2$	$S_1$	$S_0$	$A$	$S'_2$	$S'_1$	$S'_0$
0	0	0	0			
0	0	0	1			
0	0	1	0			
0	0	1	1			
0	1	0	0			
0	1	0	1			
0	1	1	0			
0	1	1	1			
1	0	0	0			
1	0	0	1			

State	Encoding
S0	000
S1	001
S2	010
S3	011
S4	100

# Moore FSM State Transition Table

Current State			Inputs	Next State		
$S_2$	$S_1$	$S_0$	$A$	$S'_2$	$S'_1$	$S'_0$
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	0	0
0	0	1	1	0	1	0
0	1	0	0	0	1	1
0	1	0	1	0	1	0
0	1	1	0	0	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	0
1	0	0	1	0	1	0

State	Encoding
S0	000
S1	001
S2	010
S3	011
S4	100

# Moore FSM Output Table

---

Current State			Output
$S_2$	$S_1$	$S_0$	$Y$
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	

# Moore FSM Output Table

---

Current State			Output
$S_2$	$S_1$	$S_0$	$Y$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1

$$Y = S_2$$

## Mealy FSM State Transition and Output Table

---

Current State		Input	Next State		Output
$S_1$	$S_0$	$A$	$S'_1$	$S'_0$	$Y$
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

State	Encoding
S0	00
S1	01
S2	10
S3	11


# Mealy FSM State Transition and Output Table

---


Current State		Input	Next State		Output
$S_1$	$S_0$	$A$	$S'_1$	$S'_0$	$Y$
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	1	1	0
1	0	1	1	0	0
1	1	0	0	0	0
1	1	1	0	1	1

State	Encoding
S0	00
S1	01
S2	10
S3	11


# Moore FSM Schematic

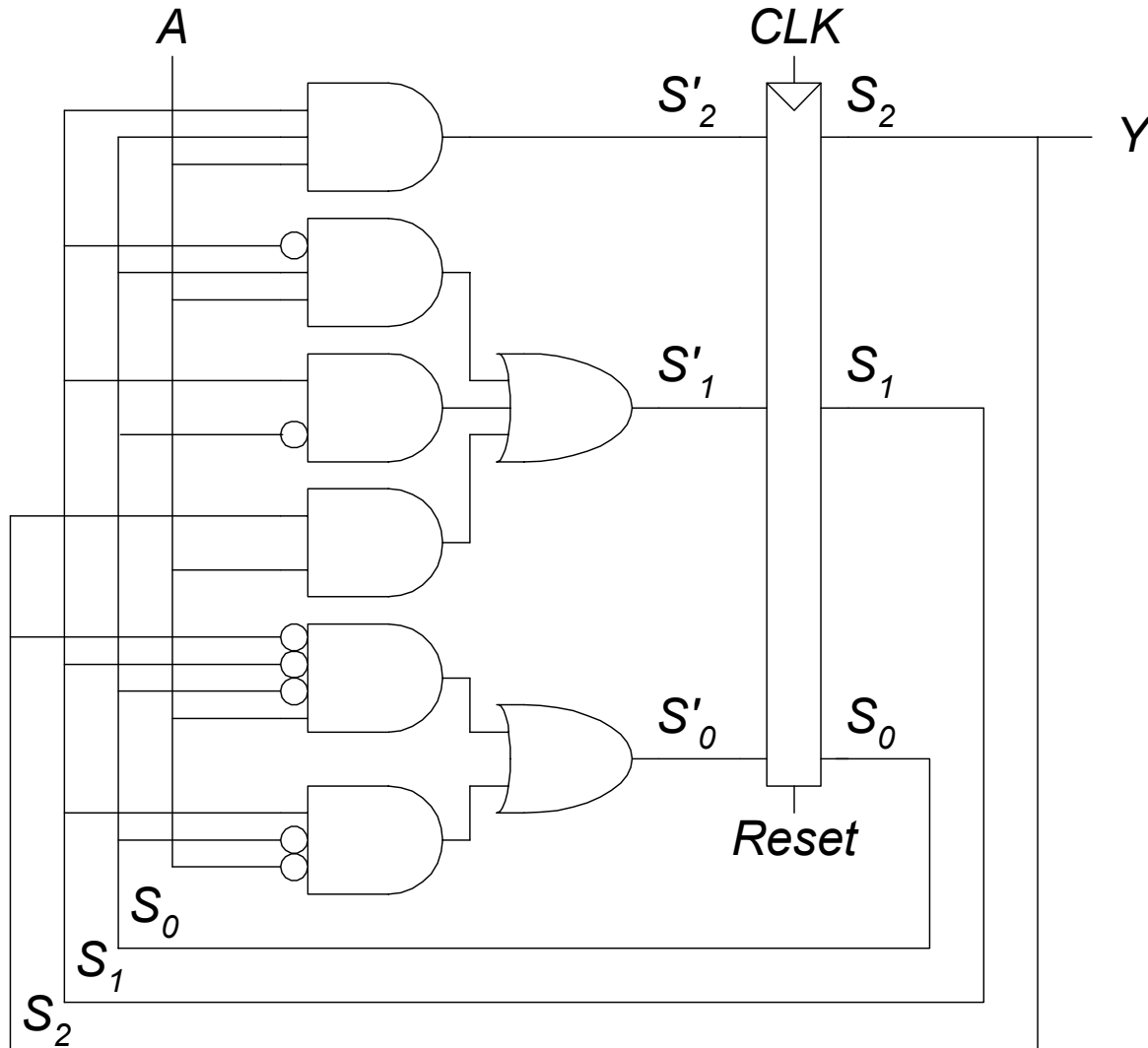

# Mealy FSM Schematic

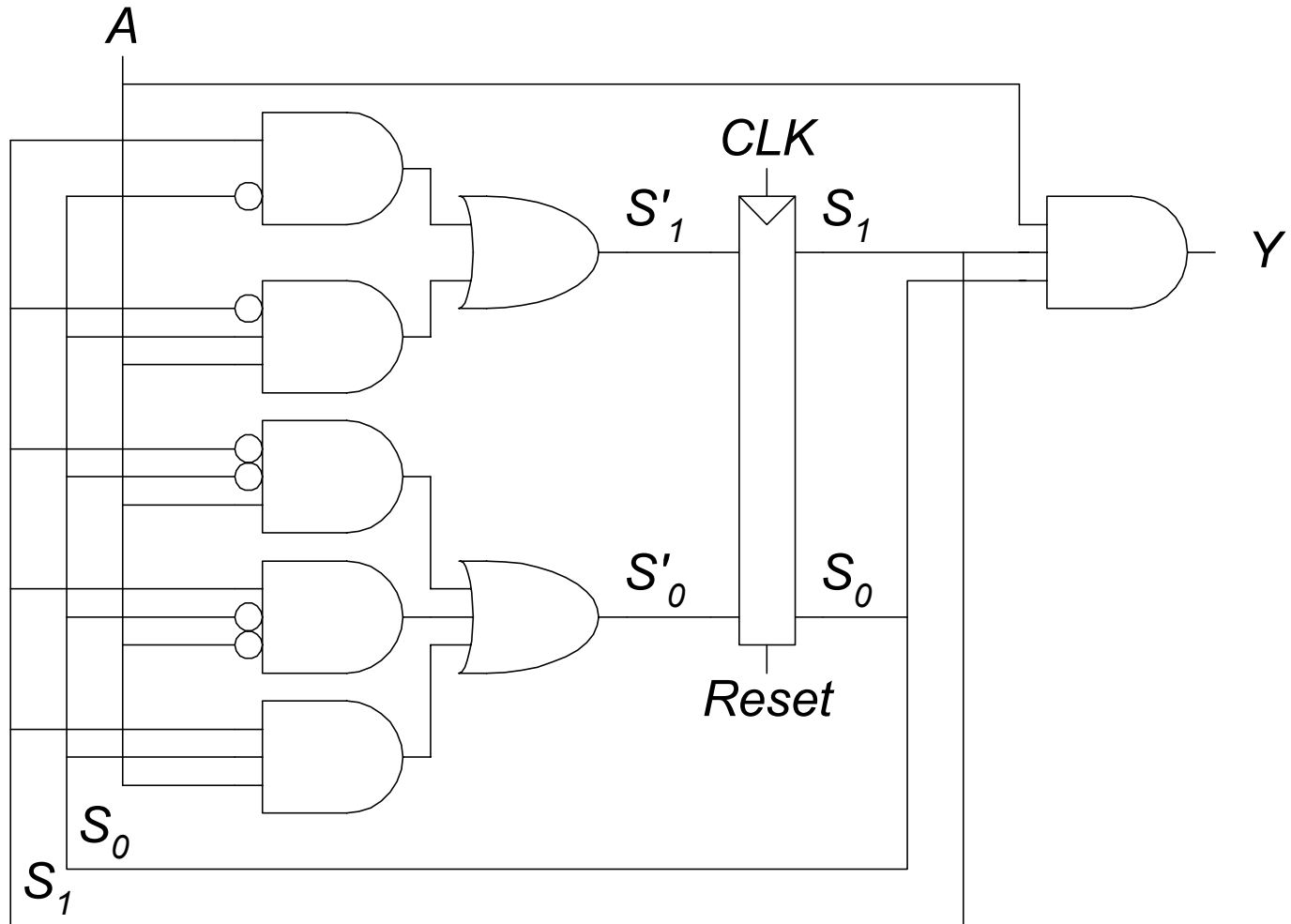

# Moore and Mealy Timing Diagram

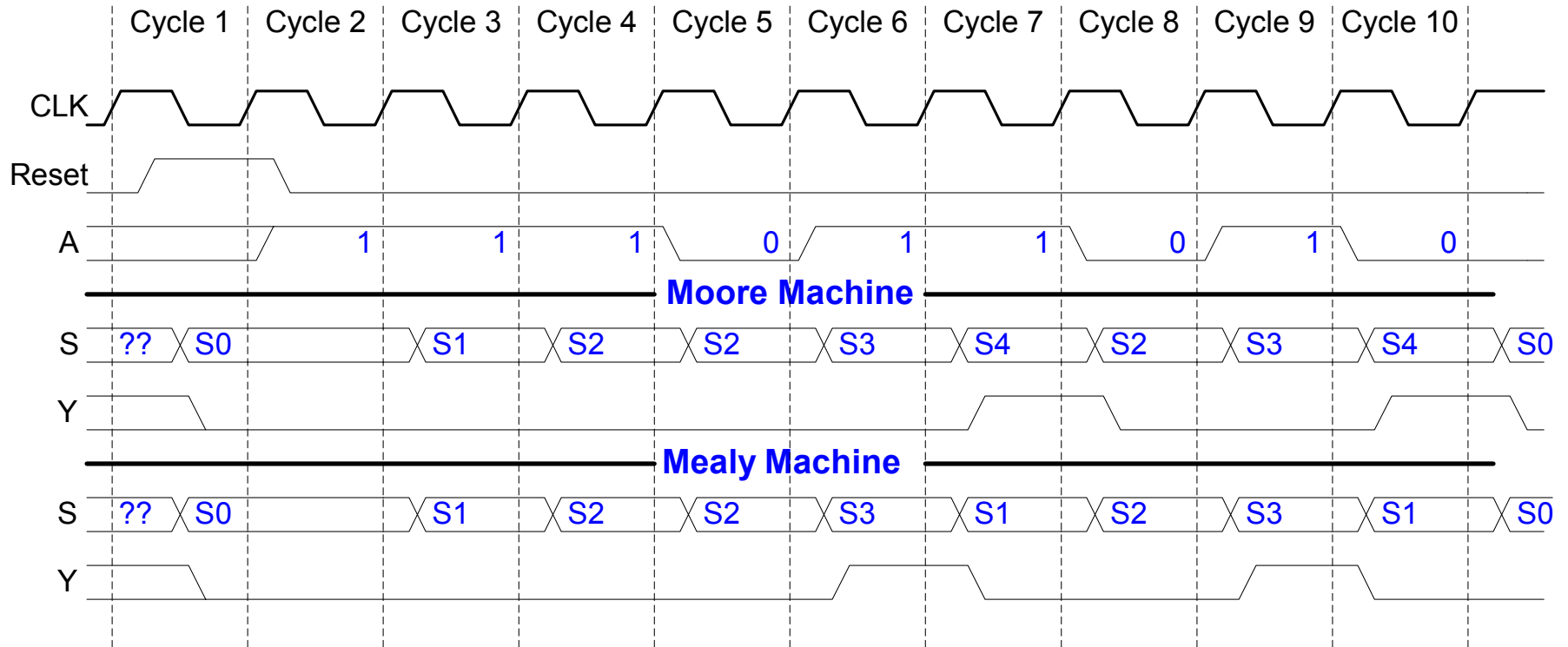


# Timing

---

- Flip-flop samples  $D$  at clock edge
- $D$  must be stable when it is sampled
- Similar to a photograph,  $D$  must be stable around the clock edge
- If  $D$  is changing when it is sampled, metastability can occur
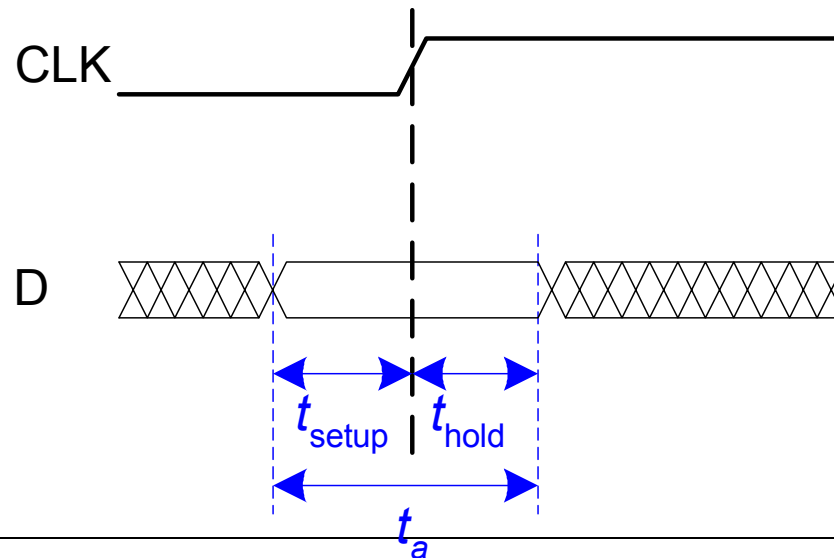
# Input Timing Constraints


- Setup time:  $t_{\text{setup}}$  = time *before* the clock edge that data must be stable (i.e. not changing)
- Hold time:  $t_{\text{hold}}$  = time *after* the clock edge that data must be stable
- Aperture time:  $t_a$  = time around clock edge that data must be stable ( $t_a = t_{\text{setup}} + t_{\text{hold}}$ )


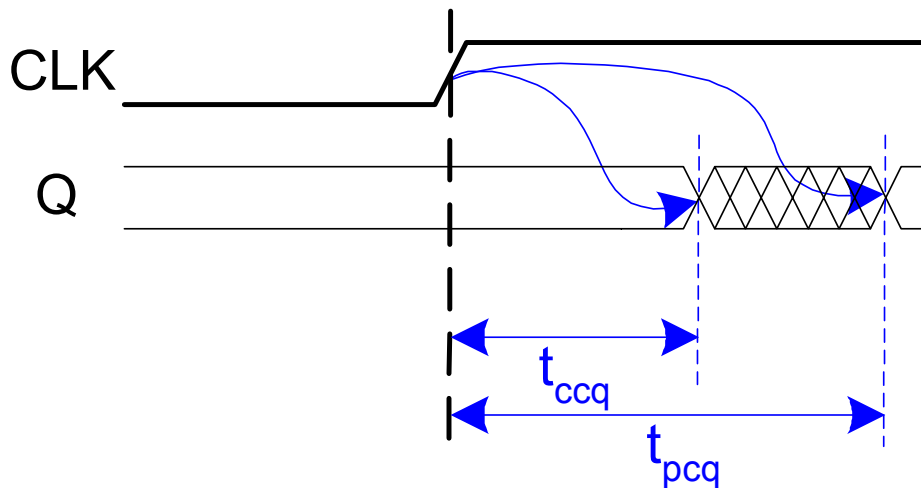
# Output Timing Constraints

---

- Propagation delay:  $t_{pcq}$  = time after clock edge that the output  $Q$  is guaranteed to be stable (i.e., to stop changing)
- Contamination delay:  $t_{ccq}$  = time after clock edge that  $Q$  might be unstable (i.e., start changing)




# Dynamic Discipline

---

- The input to a synchronous sequential circuit must be stable during the aperture (setup and hold) time around the clock edge.
- Specifically, the input must be stable
  - at least  $t_{\text{setup}}$  before the clock edge
  - at least until  $t_{\text{hold}}$  after the clock edge

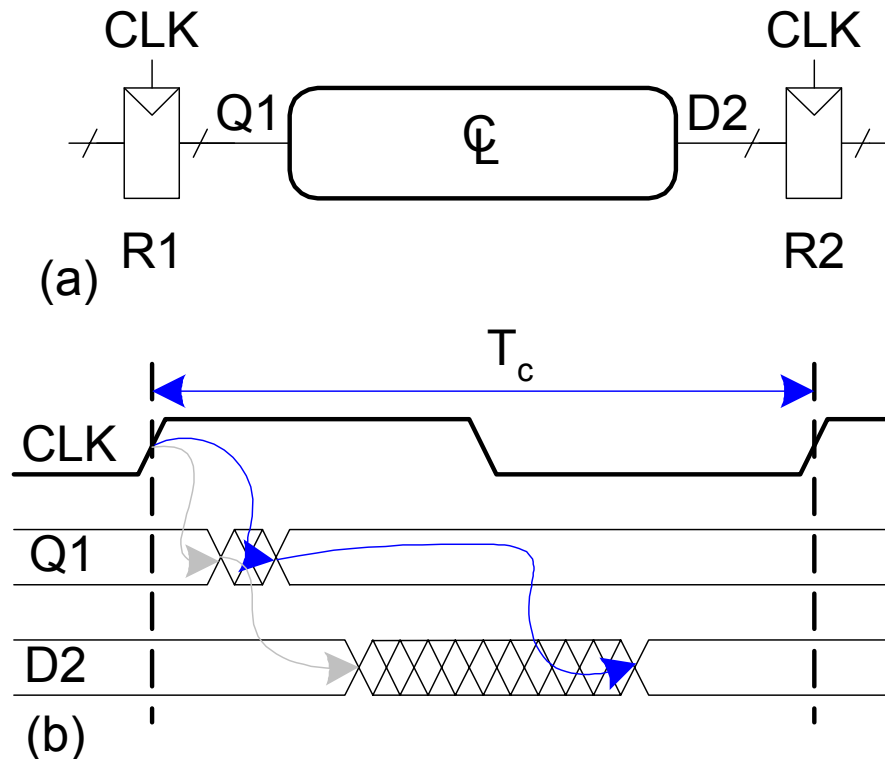
# Dynamic Discipline

- The delay between registers has a **minimum** and **maximum** delay, dependent on the delays of the circuit elements


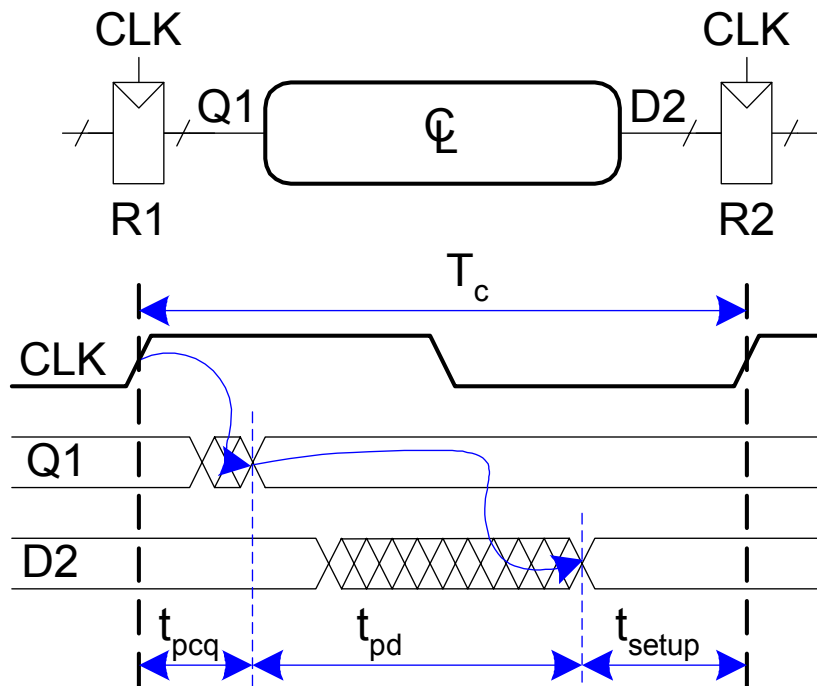
# Setup Time Constraint


- The setup time constraint depends on the **maximum** delay from register R1 through the combinational logic.
- The input to register R2 must be stable at least  $t_{\text{setup}}$  before the clock edge.



$$T_c \geq$$
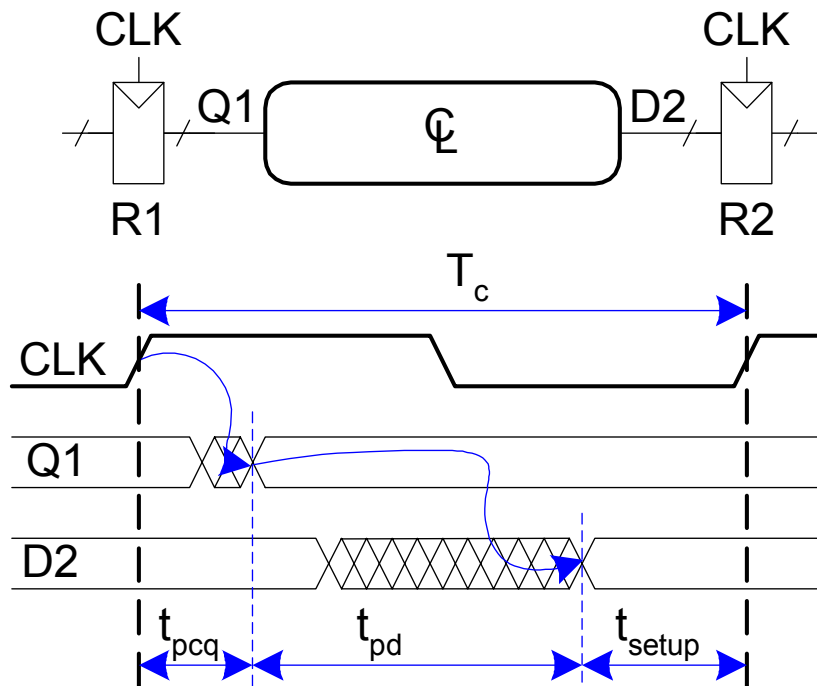
# Setup Time Constraint


- The setup time constraint depends on the **maximum** delay from register R1 through the combinational logic.
- The input to register R2 must be stable at least  $t_{\text{setup}}$  before the clock edge.



$$T_c \geq t_{pcq} + t_{pd} + t_{\text{setup}}$$
$$t_{pd} \leq$$
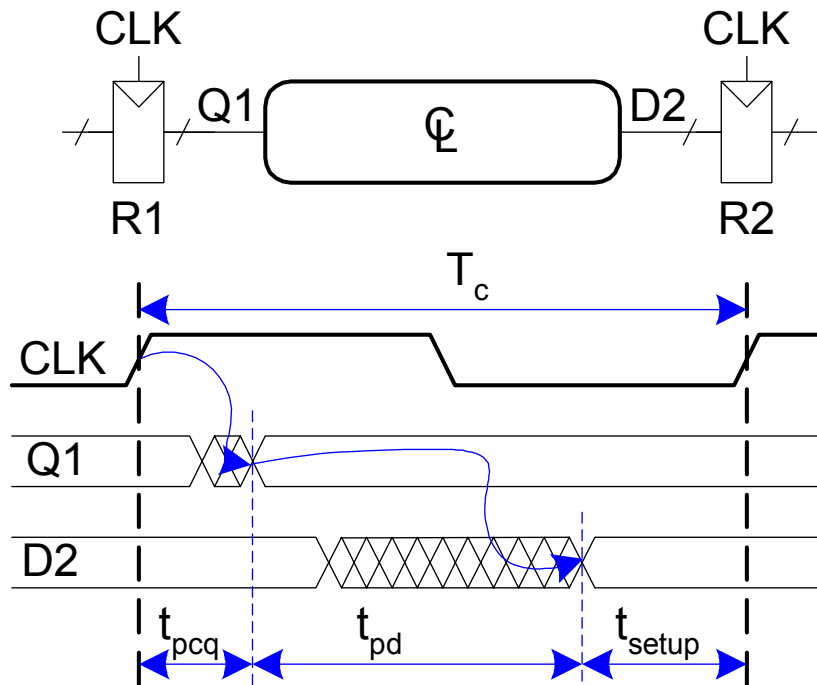
# Setup Time Constraint


- The setup time constraint depends on the **maximum** delay from register R1 through the combinational logic.
- The input to register R2 must be stable at least  $t_{\text{setup}}$  before the clock edge.



$$T_c \geq t_{pcq} + t_{pd} + t_{\text{setup}}$$
$$t_{pd} \leq T_c - (t_{pcq} + t_{\text{setup}})$$
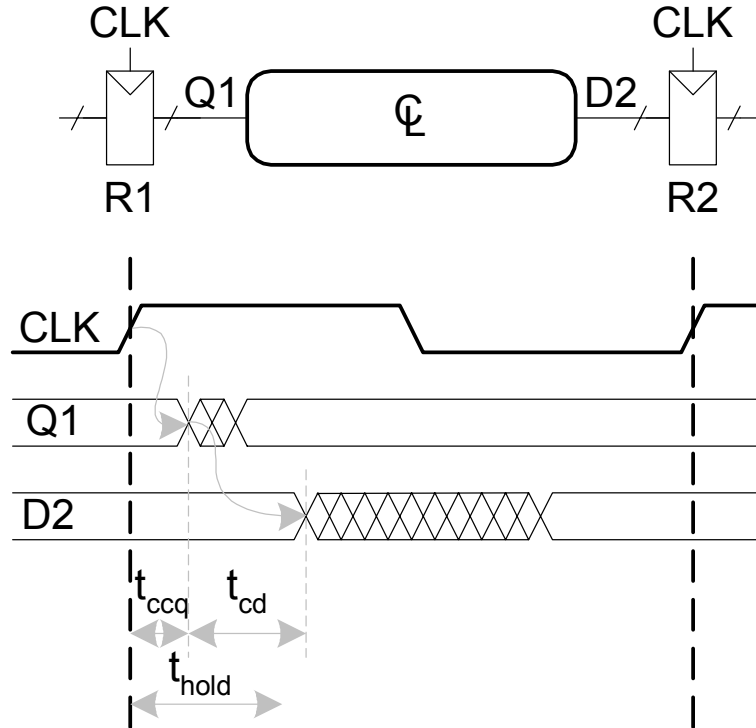
# Hold Time Constraint


- The hold time constraint depends on the **minimum** delay from register R1 through the combinational logic.
- The input to register R2 must be stable for at least  $t_{\text{hold}}$  after the clock edge.



$$t_{\text{hold}} <$$
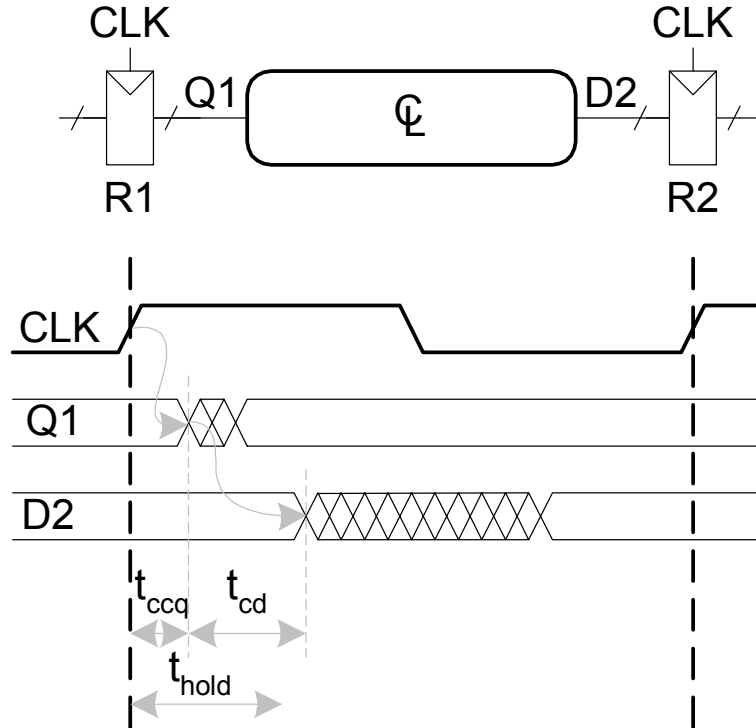
# Hold Time Constraint


- The hold time constraint depends on the **minimum** delay from register R1 through the combinational logic.
- The input to register R2 must be stable for at least  $t_{\text{hold}}$  after the clock edge.



$$t_{\text{hold}} < t_{\text{ccq}} + t_{\text{cd}}$$
$$t_{\text{cd}} >$$
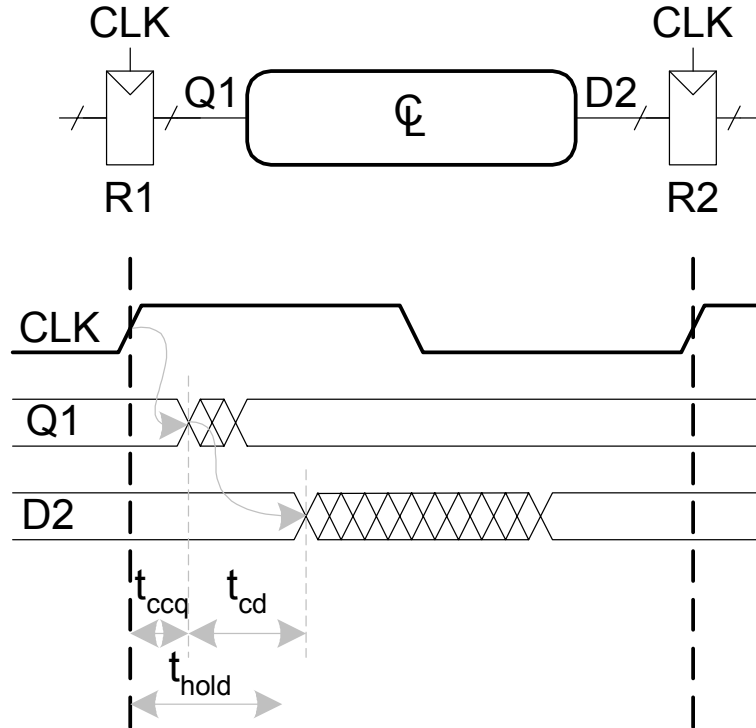
# Hold Time Constraint


- The hold time constraint depends on the **minimum** delay from register R1 through the combinational logic.
- The input to register R2 must be stable for at least  $t_{\text{hold}}$  after the clock edge.



$$t_{\text{hold}} < t_{\text{ccq}} + t_{\text{cd}}$$

$$t_{\text{cd}} > t_{\text{hold}} - t_{\text{ccq}}$$

# Timing Analysis

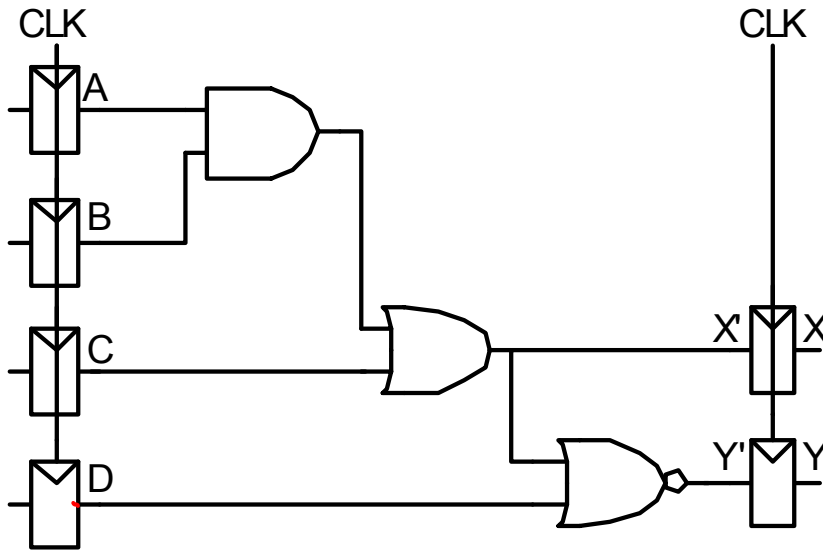

## Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

per gate

$$\left[ \begin{array}{l} t_{pd} = 35 \text{ ps} \\ t_{cd} = 25 \text{ ps} \end{array} \right.$$

$$T_{pd}$$

$$t_{cd} =$$

Setup time constraint:


$$T_c \geq$$

$$f_c = 1/T_c =$$

Hold time constraint:

$$t_{ccq} + t_{cd} > t_{\text{hold}} ?$$

# Timing Analysis

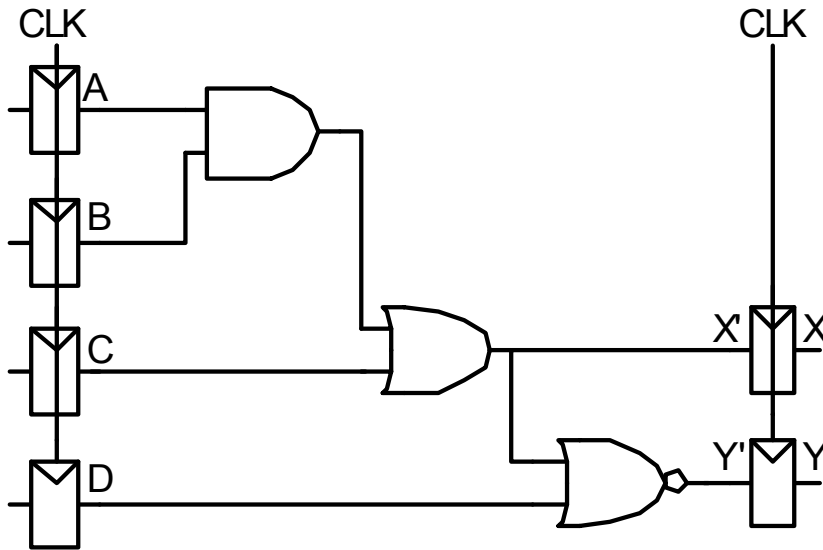

## Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

per gate

$$\left[ \begin{array}{l} t_{pd} = 35 \text{ ps} \\ t_{cd} = 25 \text{ ps} \end{array} \right.$$

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 25 \text{ ps}$$

Setup time constraint:

$$T_c \geq (50 + 105 + 60) \text{ ps} = 215 \text{ ps}$$

$$f_c = 1/T_c = 4.65 \text{ GHz}$$


Hold time constraint:

$$t_{ccq} + t_{cd} > t_{\text{hold}} ?$$

$$(30 + 25) \text{ ps} > 70 \text{ ps} ? \text{ No!}$$

# Fixing Hold Time Violation

Add buffers to the short paths:

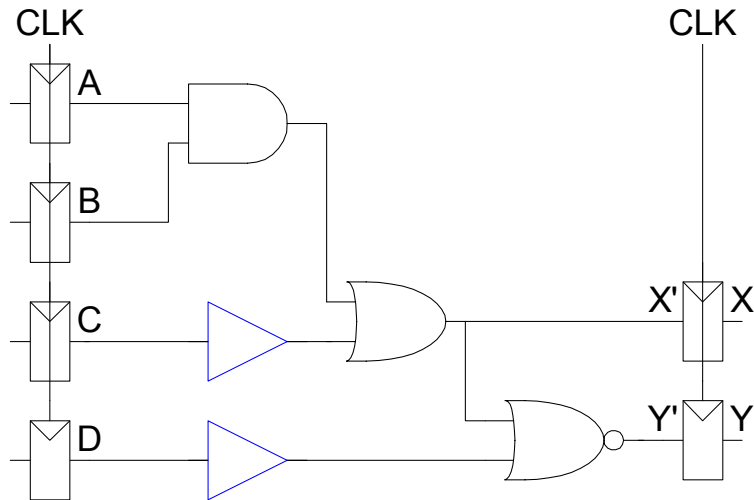

$$t_{pd} =$$

$$t_{cd} =$$

Setup time constraint:

$$T_c \geq$$

$$f_c =$$

## Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

per gate


$$\left[ \begin{array}{l} t_{pd} = 35 \text{ ps} \\ t_{cd} = 25 \text{ ps} \end{array} \right.$$

Hold time constraint:

$$t_{ccq} + t_{cd} > t_{\text{hold}} ?$$

# Fixing Hold Time Violation

Add buffers to the short paths:

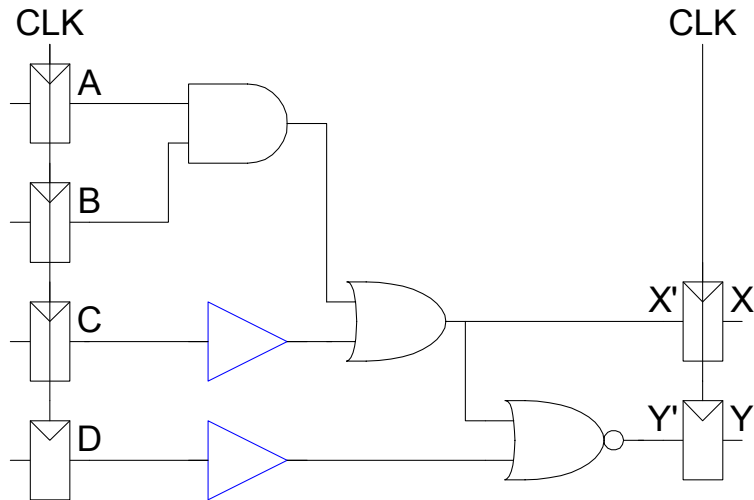

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 2 \times 25 \text{ ps} = 50 \text{ ps}$$

Setup time constraint:

$$T_c \geq (50 + 105 + 60) \text{ ps} = 215 \text{ ps}$$

$$f_c = 1/T_c = 4.65 \text{ GHz}$$

## Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

per gate

$$\left[ \begin{array}{l} t_{pd} = 35 \text{ ps} \\ t_{cd} = 25 \text{ ps} \end{array} \right.$$

Hold time constraint:

$$t_{ccq} + t_{cd} > t_{\text{hold}} ?$$

$$(30 + 50) \text{ ps} > 70 \text{ ps} ? \text{ Yes!}$$